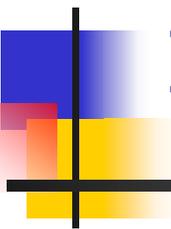


# Laboratory Exercises for Analog Circuits and Electronics as Hardware Homework with Student Laptop Computer Instrumentation




---

Marion O. Hagler

Department of Electrical and Computer  
Engineering

Mississippi State, MS 39762 USA

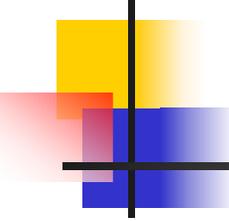
[hagler@ece.msstate.edu](mailto:hagler@ece.msstate.edu)


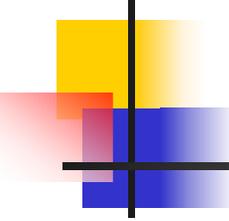
# Introduction

---

- Since 1999, all ECE undergraduate students at MSU have laptop computers
- In spring 2005, first course in electronic circuits will require hardware homework
  - Students construct circuits at home
  - Measure circuit performance with audio capability of laptops as oscilloscope, spectral analyzer, and signal generator



# Basic Approach


---

By pair wise comparison of

- Analysis
- Measurement
- Simulation

students

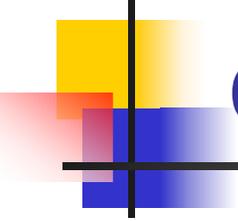- Deploy complex, intensely interactive, learning environments
- Learn to self-assess their work




# Circuits with inductors and capacitors

---

- Student laptop functions as:
  - Signal generator
  - Oscilloscope
  - Spectrum analyzer
- Software (~US\$90):
  - Realtime Analyzer (DSSF3 Light version)
  - <http://www.ymec.com/products/dssf3e/>



# Circuits with inductors and capacitors

- Simple example: RC low pass filter

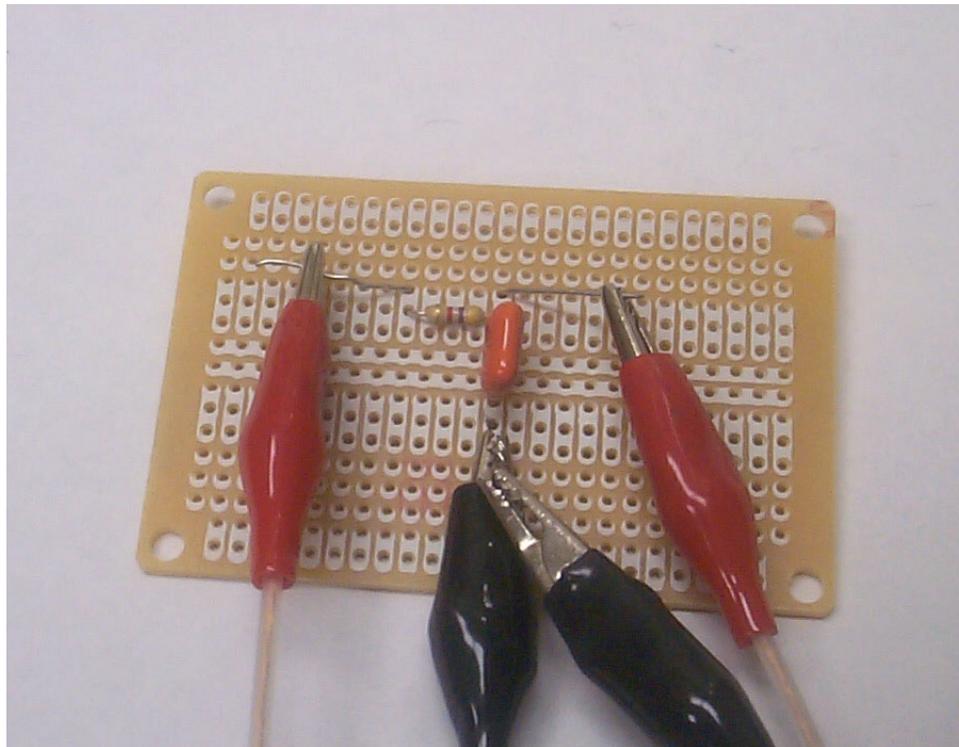

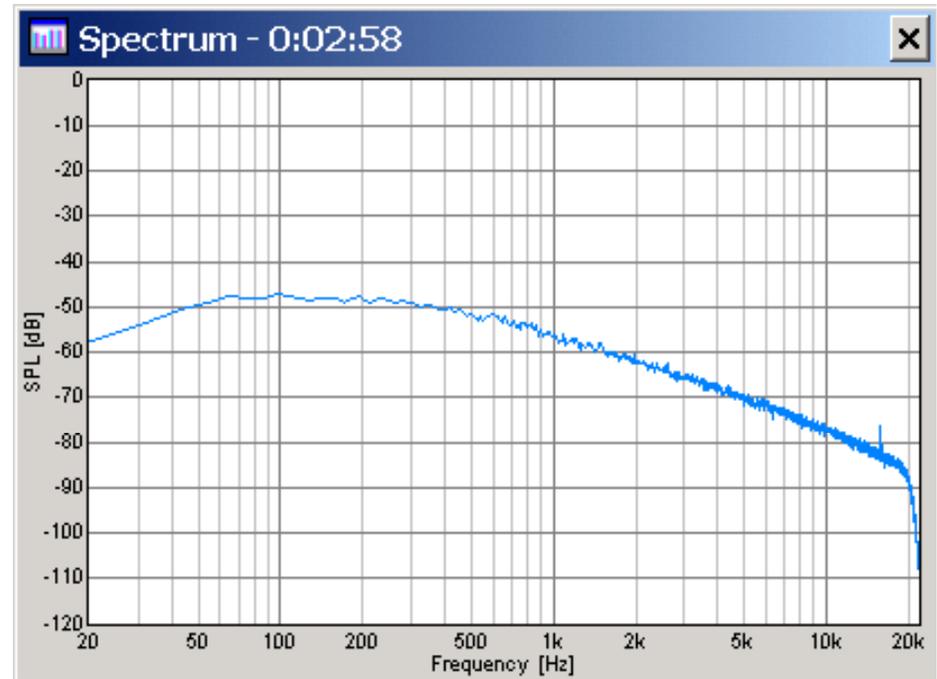
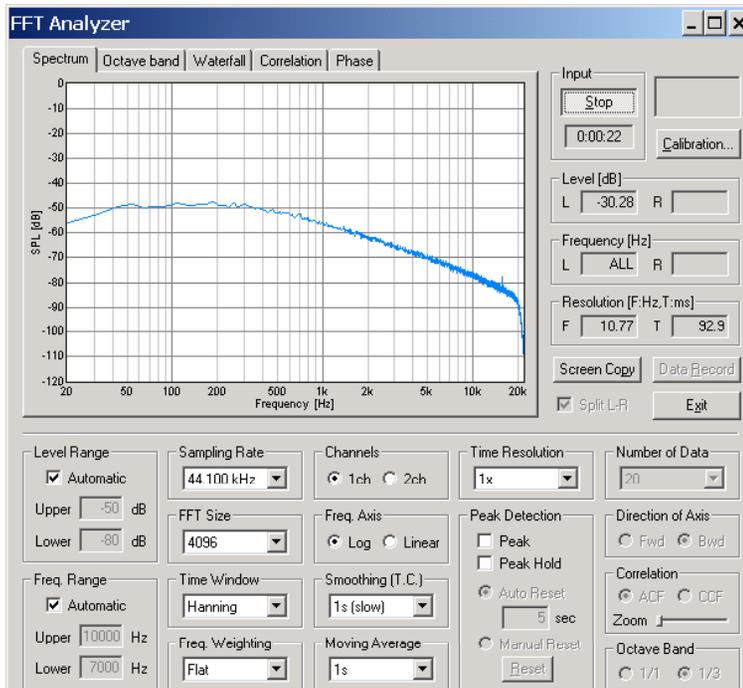
# RC low pass filter: white noise spectral response

- $R = 4700\Omega$ ,  $C = 0.1\mu\text{F}$ ,  $f_c \approx 340\text{ Hz}$



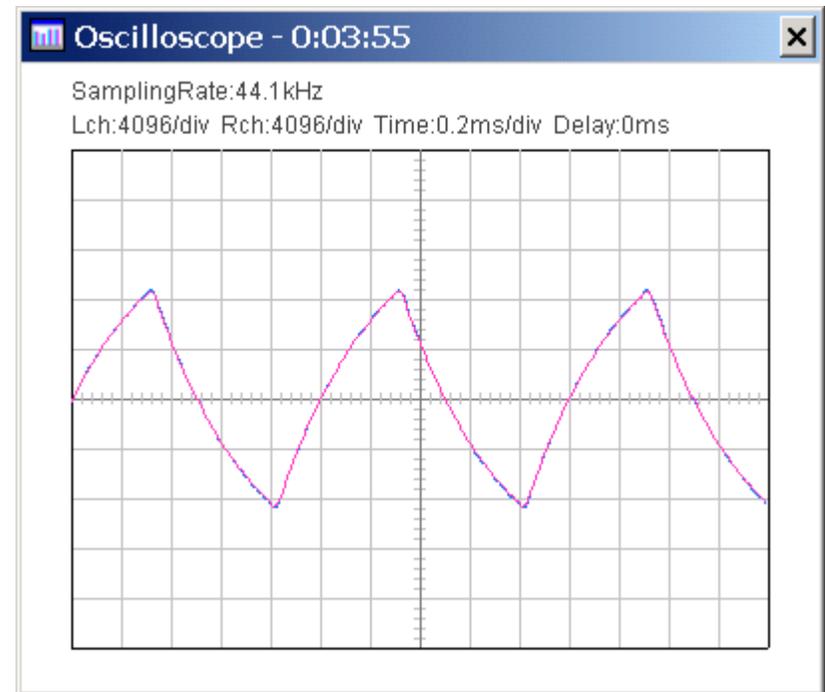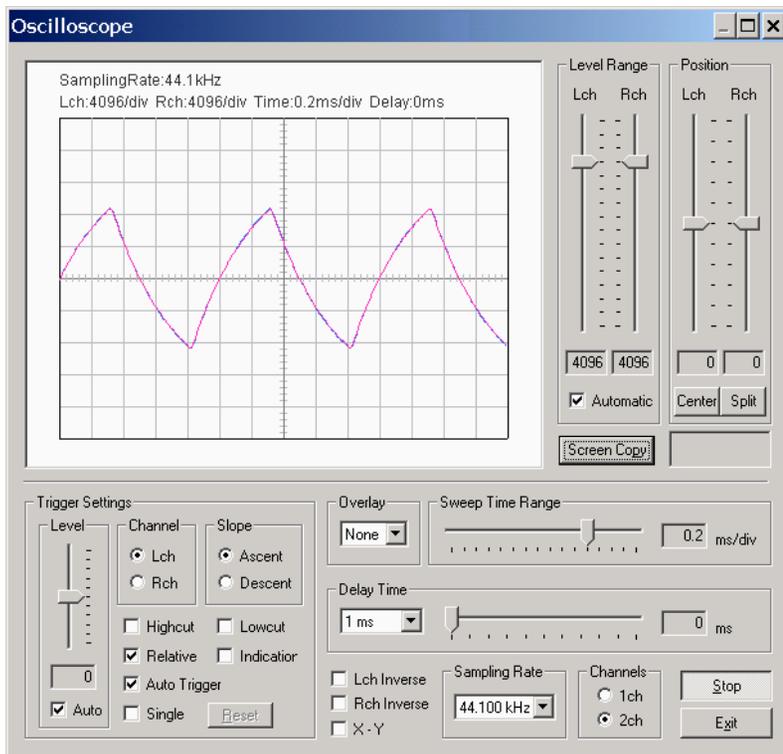
# RC low pass filter: 500 Hz square wave response

- $R = 4700\Omega$ ,  $C = 0.1\mu\text{F}$ ,  $f_c \approx 340\text{ Hz}$




# RC low pass filter: square wave and white noise inputs

1000 Hz square wave

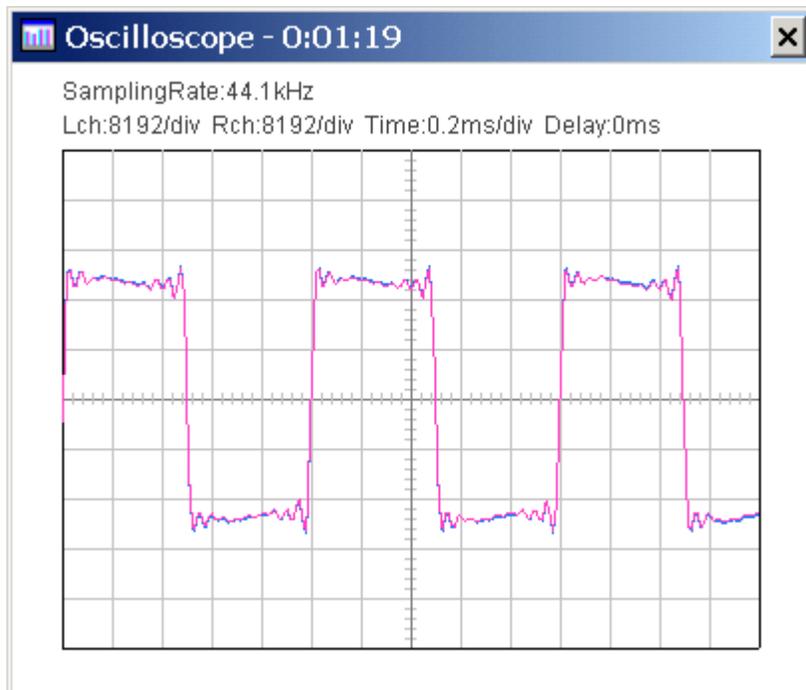


white noise

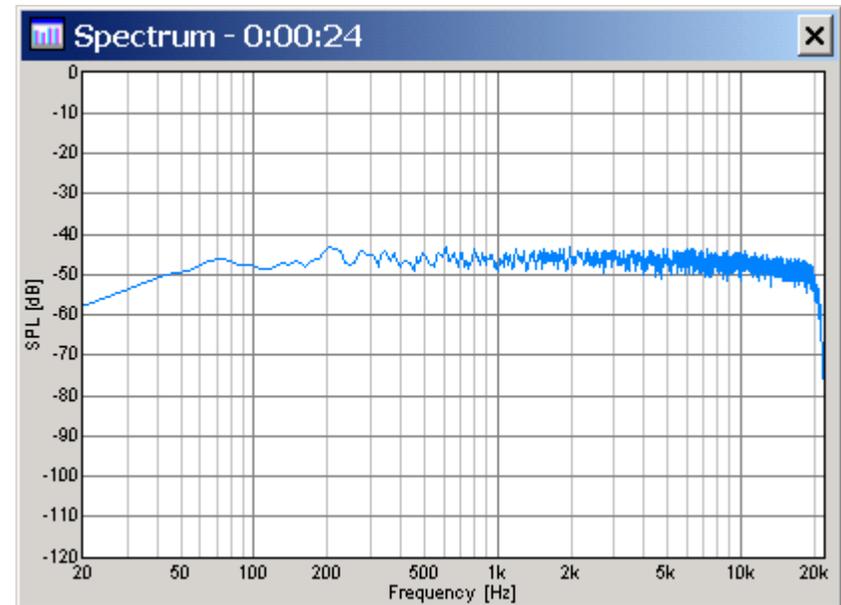

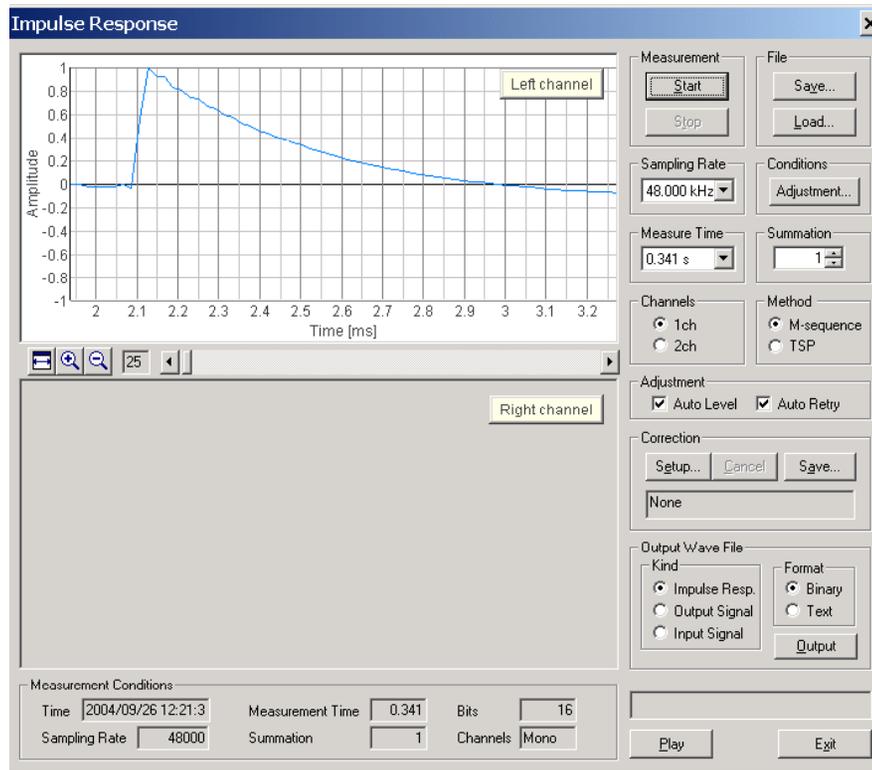
# RC low pass filter: impulse response


- $R = 4700\Omega$ ,  $C = 0.1\mu\text{F}$ ,  $RC = 0.47 \text{ msec}$



# Non-inverting op amp configuration

- Op amp GBW  $\approx 1$  MHz

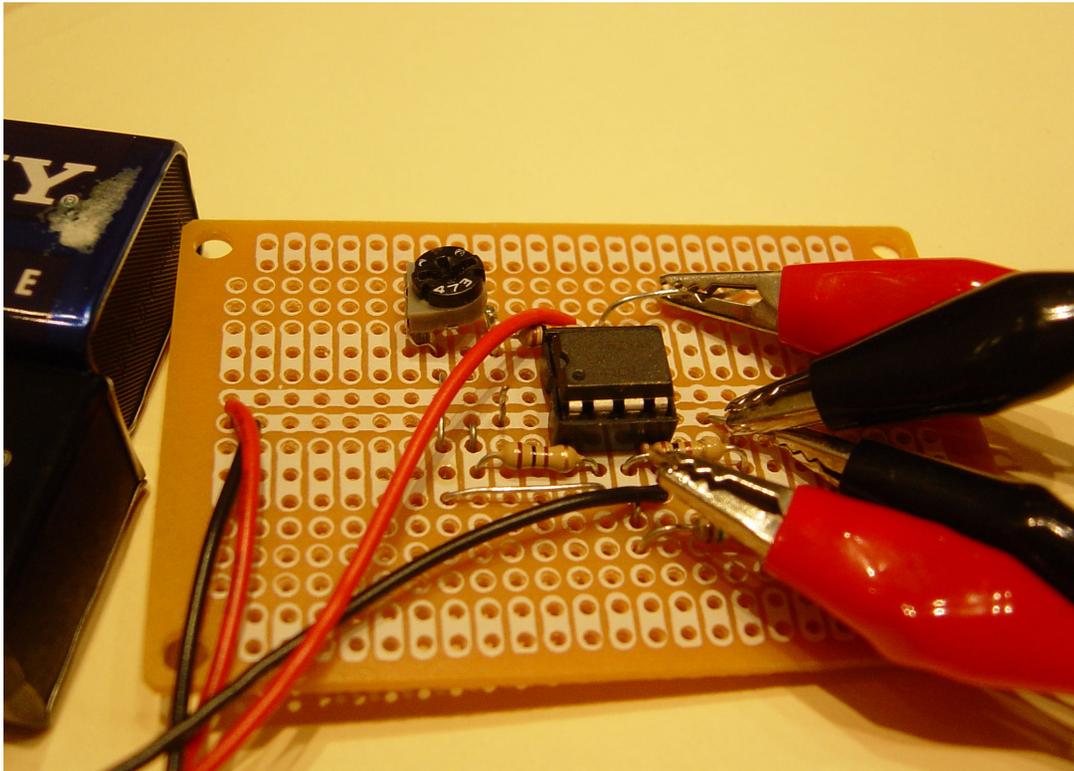

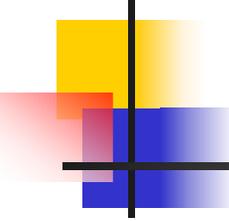

# Non-inverting op amp configuration

---

- Analysis:

- Gain without feedback: 
$$A = A_{LF} \frac{1}{1 + j \frac{f}{f_{BW}}}$$

- With feedback: 
$$G = G_{LF} \frac{1}{1 + j \frac{f}{\frac{A_{LF}}{G_{LF}} f_{BW}}}$$


- In both cases: 
$$GBW = A_{LF} f_{BW}$$

- Feedback conserves GBW


# Non-inverting op amp configuration

## ■ Response when $G = 96$


Measured input:

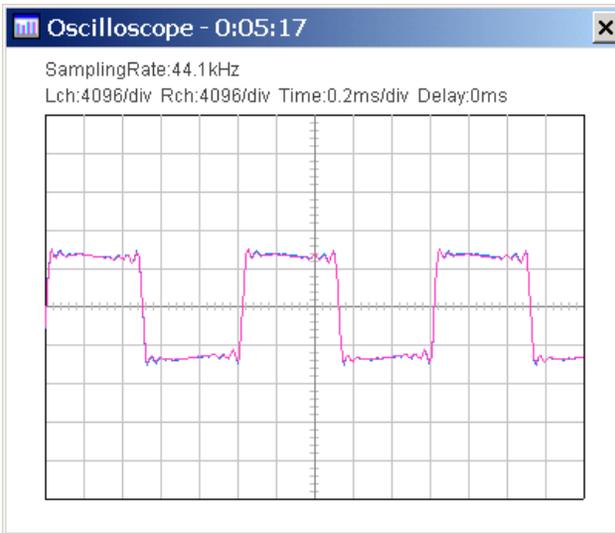

Measured output:

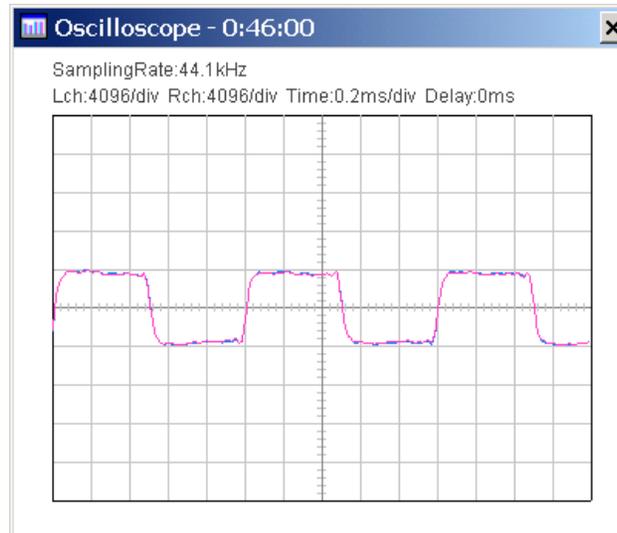


Simulation:

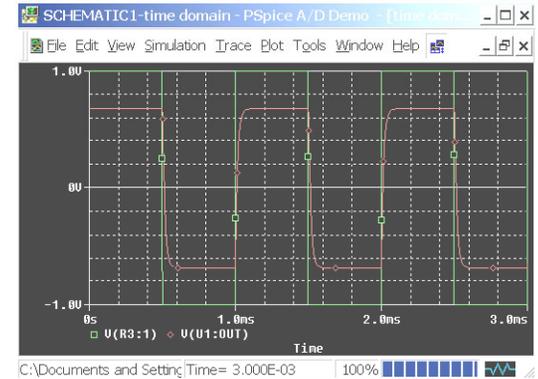


# Non-inverting op amp configuration

## ■ Response when $G = 342$


Measured input:

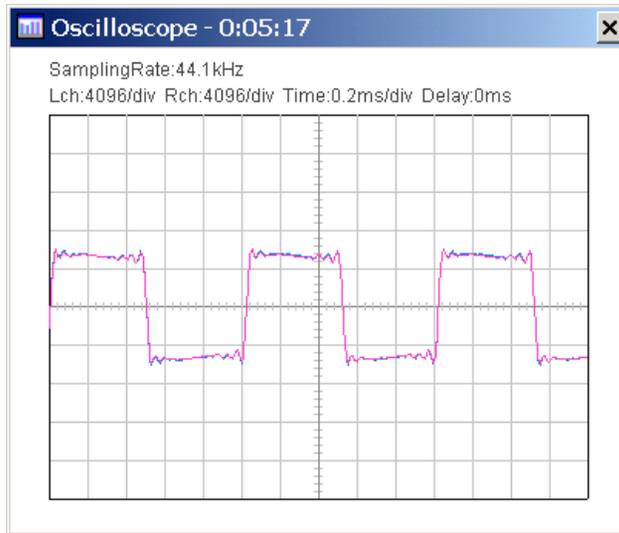

Measured output:

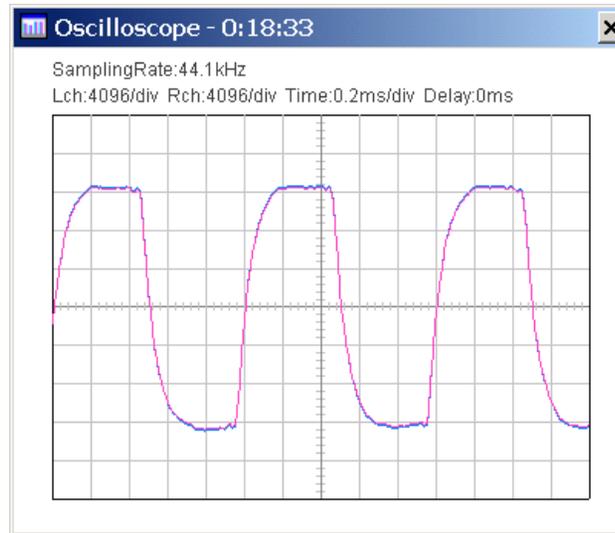


Simulation:

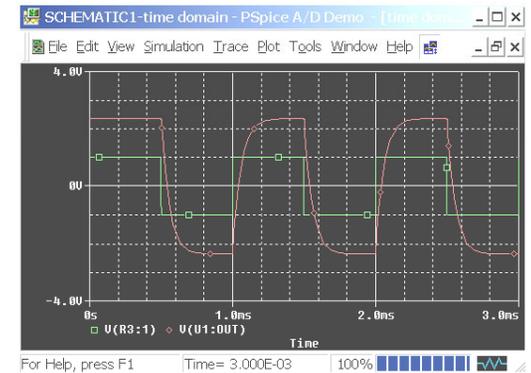


# Non-inverting op amp configuration

## ■ Response when $G = 535$


Measured input:

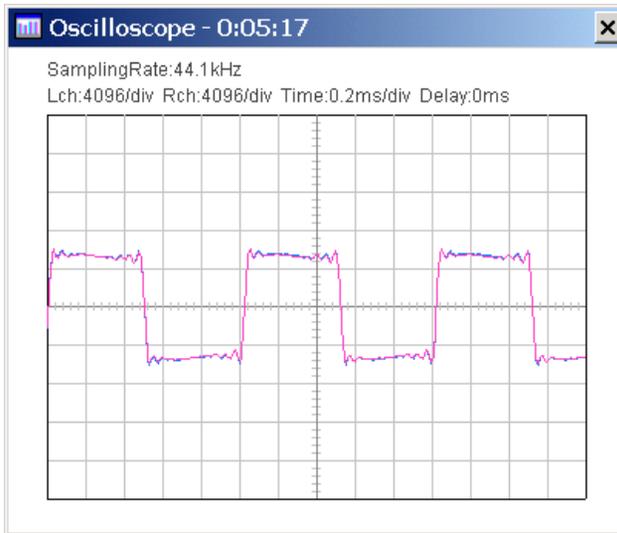

Measured output:

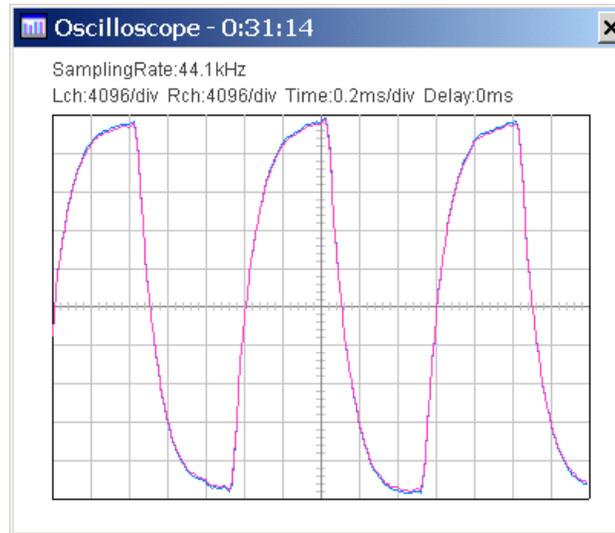

Simulation:

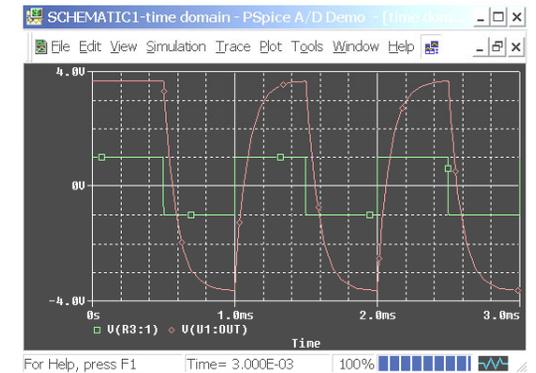

# Non-inverting op amp configuration

## ■ Spectral response:

G = measured (analytical)

G = 112 (102)

BW = 7 kHz

GBW = 786kHz

G = 399 (353)




BW = 2.2 kHz

GBW = 877 kHz

G = 563 (551)


BW = 1.6 kHz

GBW = 901 kHz

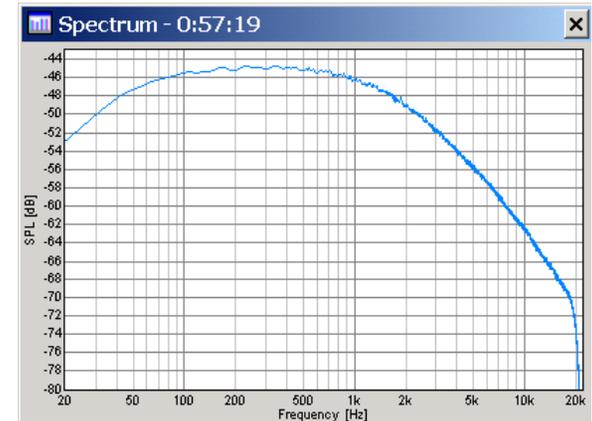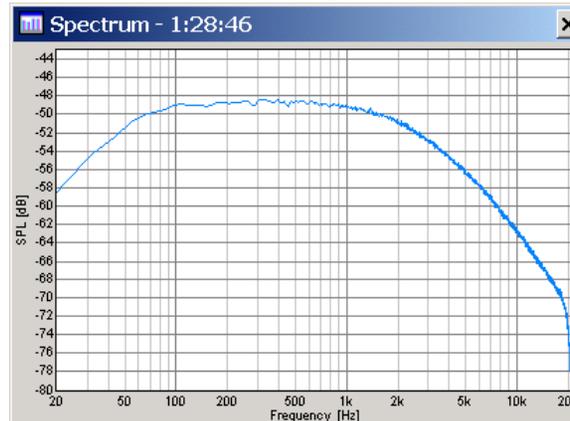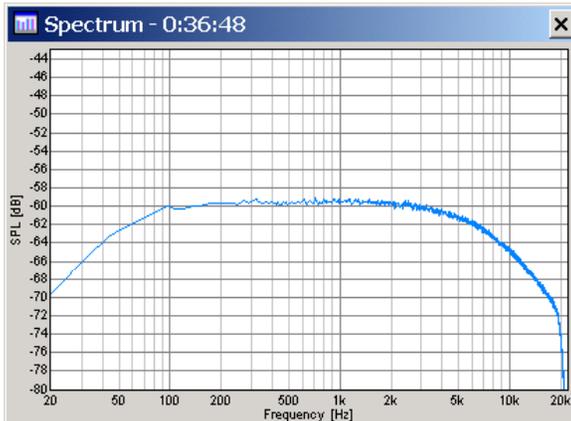
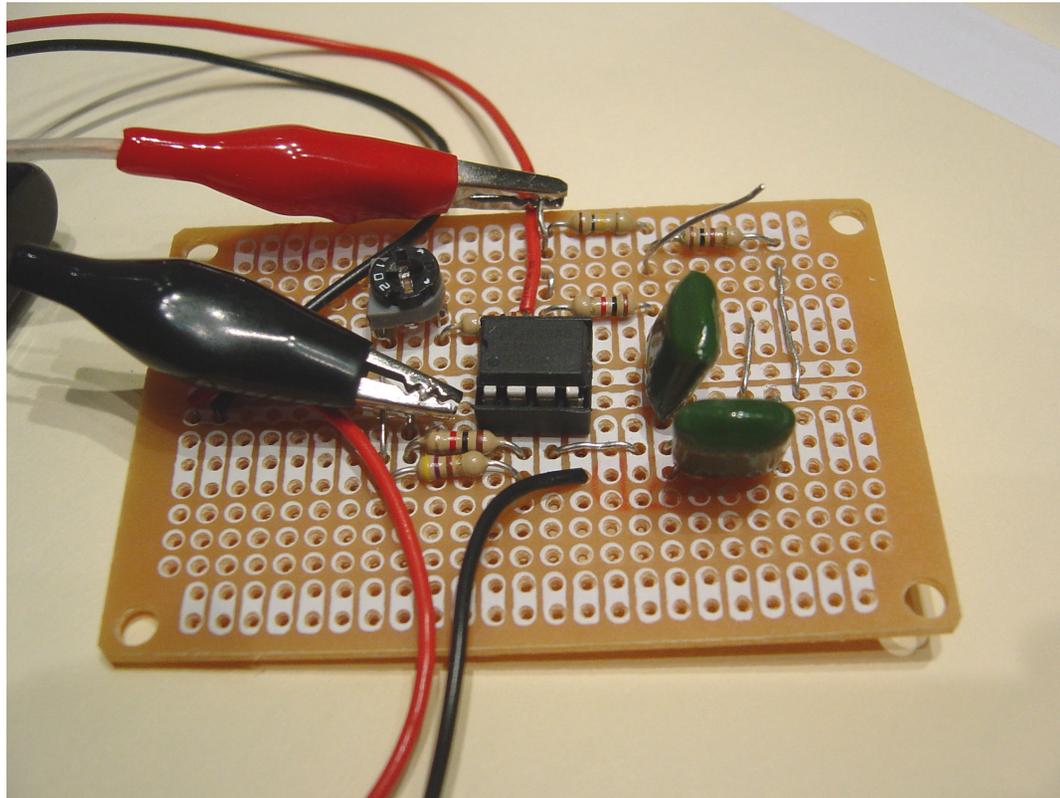
# Wien bridge op amp oscillator: $f = 1592 \text{ Hz}$

- $R = 1000\Omega$ ,  $C = 0.1\mu\text{F}$ ,  $f = 1592 \text{ Hz}$





# Wienbridge op amp oscillator: $f = 1592 \text{ Hz}$



$$G = 1.025$$

$$G = 1.030$$

Waveform:

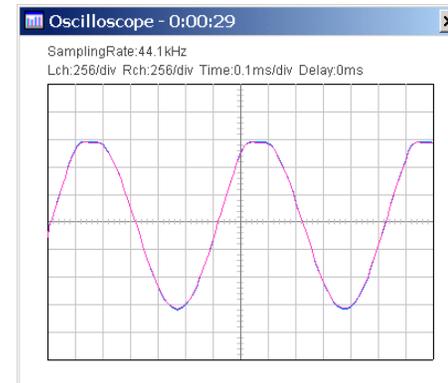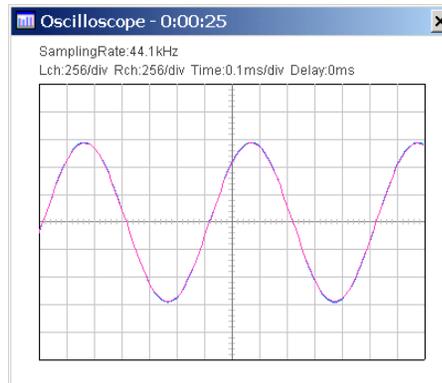

Spectrum:

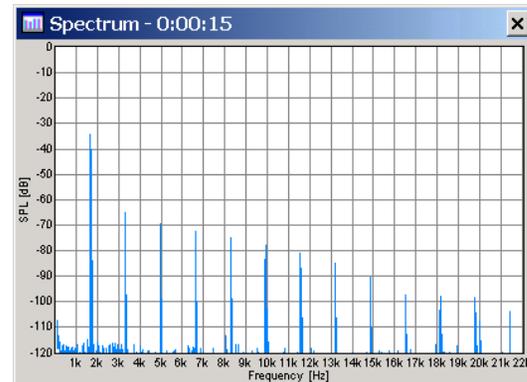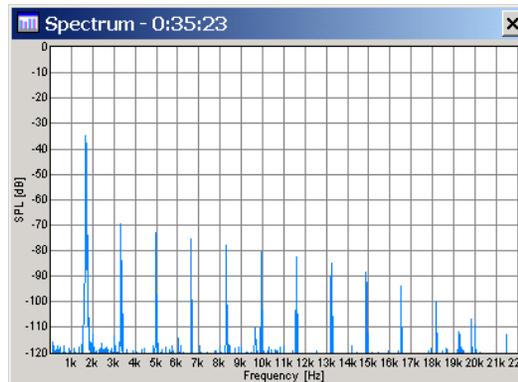


# Wienbridge op amp oscillator: $f = 1592 \text{ Hz}$

$$G = 1.025$$

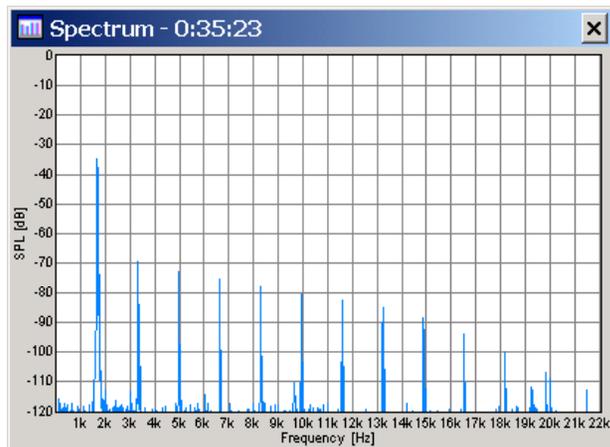
## Measured spectrum

(unequal battery volts;  
even harmonics)



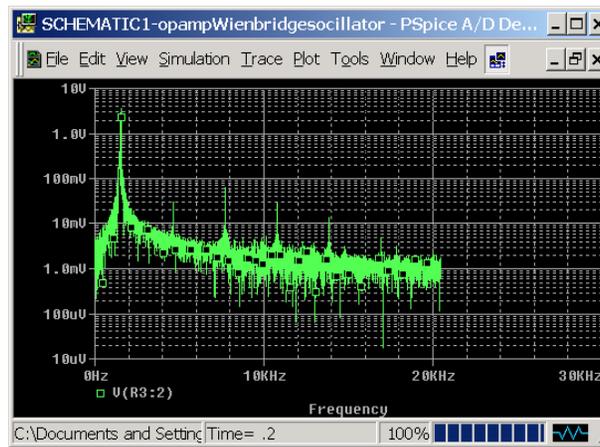
## Simulated spectrum

(equal battery volts;  
no even harmonics)



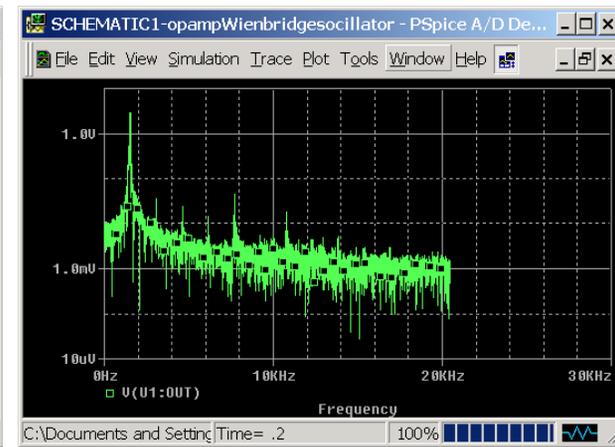
## Simulated spectrum

(unequal battery volts;  
even harmonics)


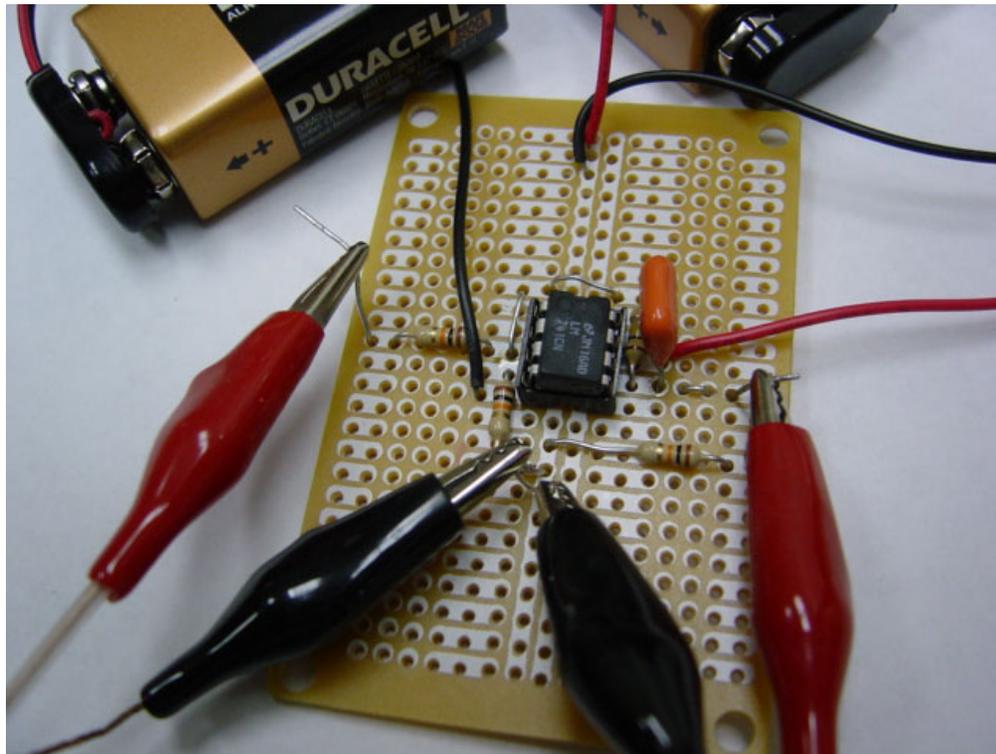
# Op amp inverting integrator


- $R = 10,000\Omega$ ,  $C = 10\text{nF}$



# Op amp inverting integrator


- Input signal

(2000 Hz square wave)

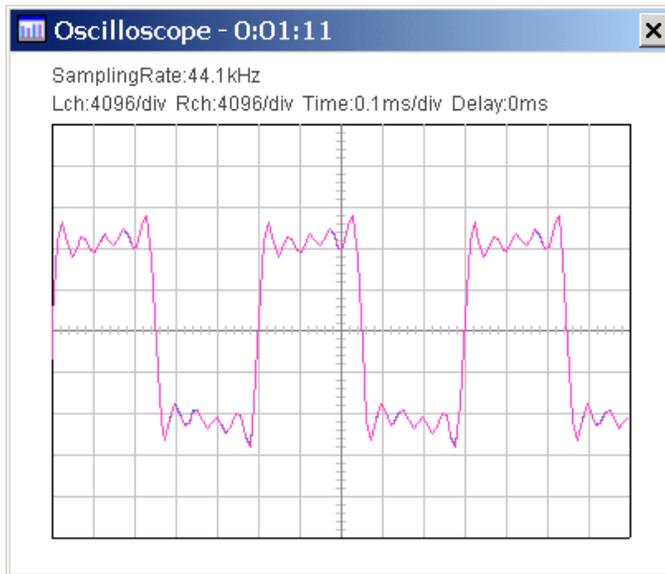

## Output signal

(2000 Hz triangular wave)

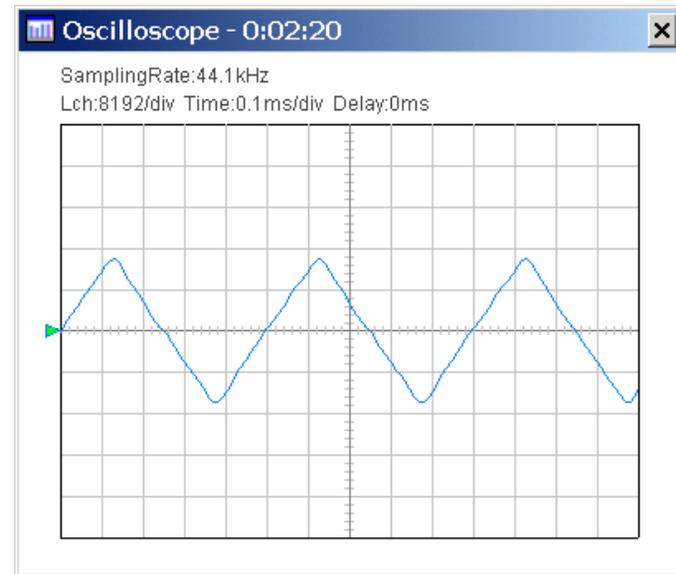


# Resistive circuits


- Students purchase and use an inexpensive (<US\$25) digital multimeter for measurements


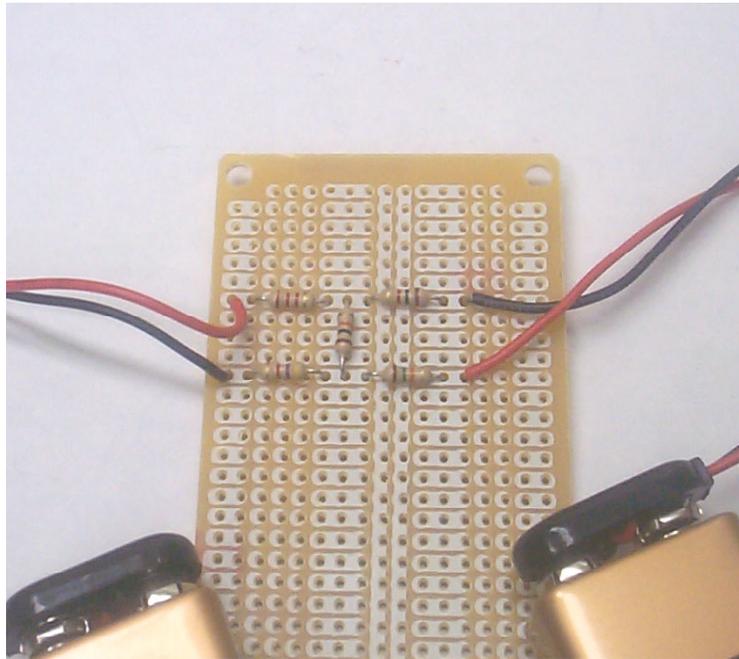
# Two loop, 5 resistor circuit

- Resistors: 1k, 2.2k, 4.7k, 10k, 15k
- Batteries: 9V, 9V



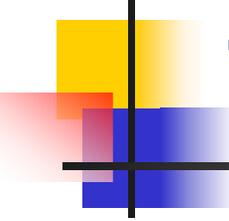


# Two loop five resistor circuit

---

- Write mesh and node equations and solve with MATLAB
- Simulate circuit with OrCAD PSpice
- Measure circuit voltages and currents with digital multimeter
- Interactive learning: comparison of measurements and calculations

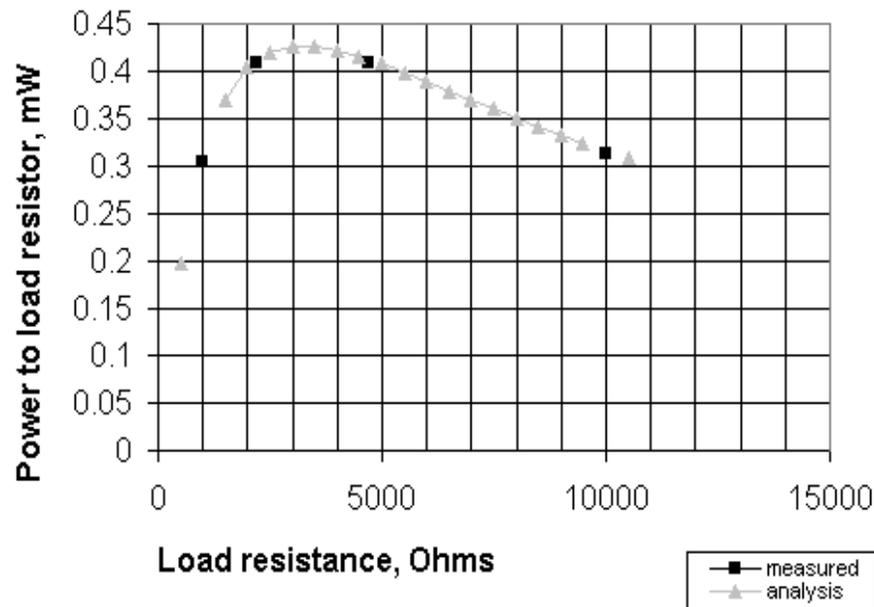
# Two loop five resistor circuit

- Plot of the power dissipated in the load resistor vs. its resistance:




# R-2R digital-to-analog converter


$R = 5000\Omega$

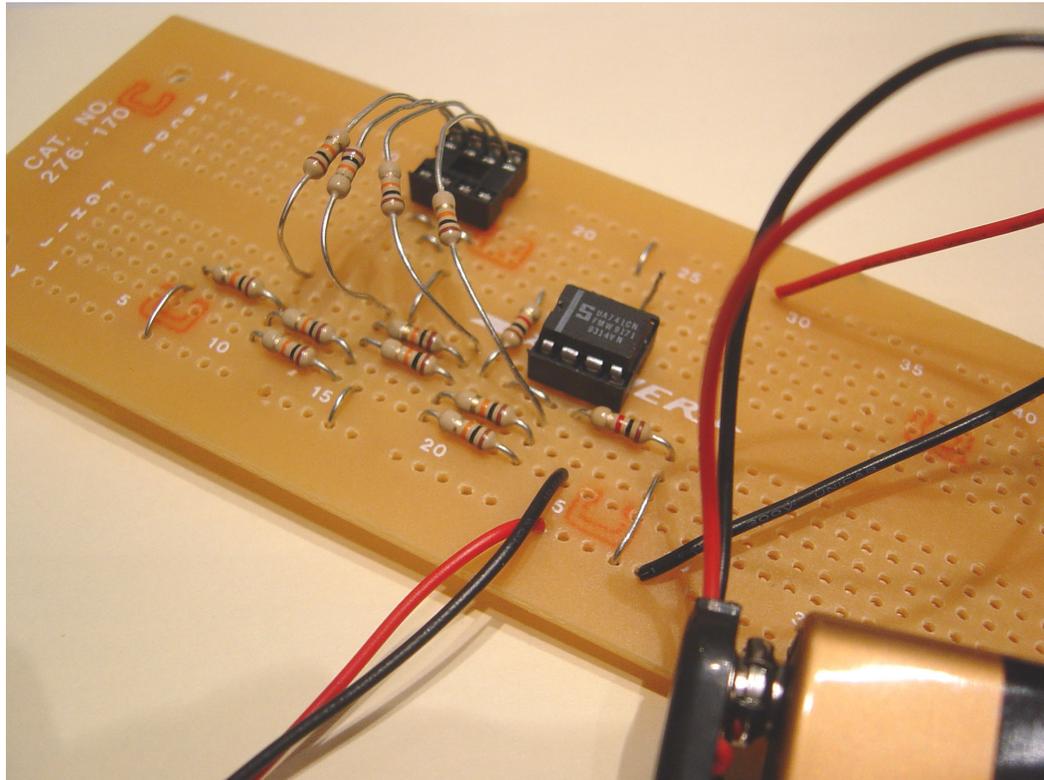

# BJT RS latch

- $R = 10k\Omega$

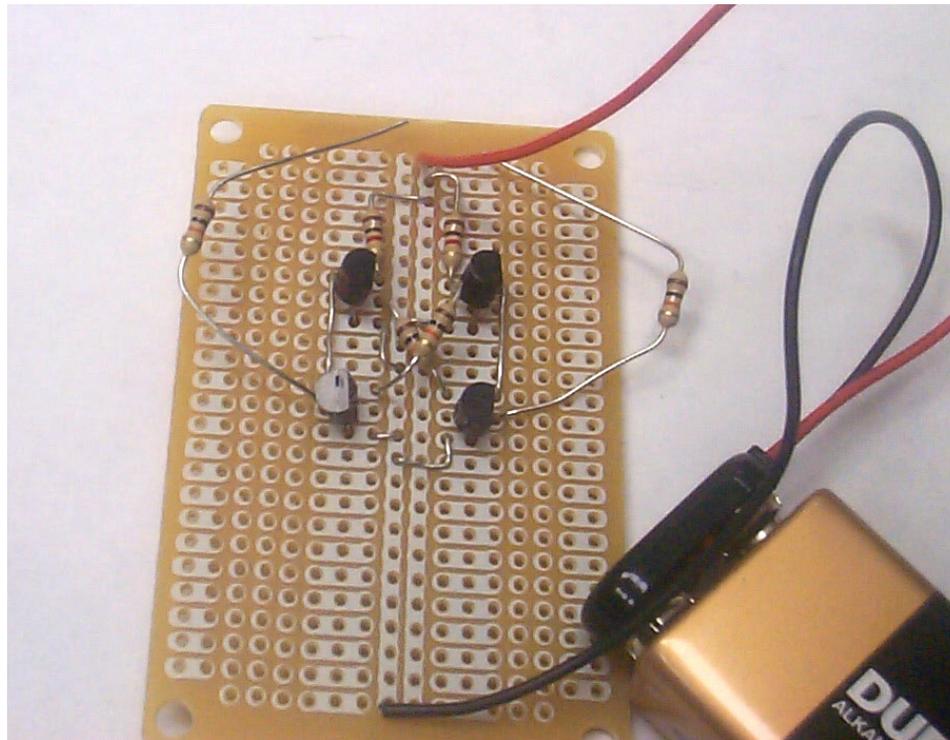

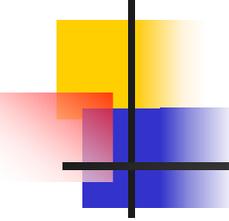


# Discussion and Conclusion

## Approximate parts list

Students already have bought shaded parts and used them for hardware homework in a first year course.

Part description	RadioShack part number	Price SUS
15-Range Digital Multimeter, with battery	22-810	23.48
1/4 Watt Resistor Assortment	271-308	6.29
9V Rectangular Battery (2)	23-875	6.58
9V Battery Snap Connectors	270-324	2.59
Adjustable resistor, 10k Ohms	271-282	1.29
0.01 $\mu$ F Capacitor (2)	272-1051	2.38
0.1 $\mu$ F Capacitor (2)	272-1053	2.38
741 Operational Amplifier IC	276-007	0.99
General Purpose IC PC Board (5)	276-150	8.95
8-Pin IC sockets (2 packages)	276-1995	1.38
Shielded Cables, 1/8" phone plug to alligator clips (2)	42-2421	6.58
Long-Nose Mini Pliers	64-2953	4.99
Soldering Pencil, 15-Watt	64-2051	8.39
0.032" Rosin Core Solder	64-017	1.59
Total		77.86

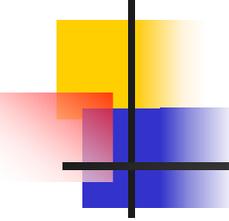

# Discussion and Conclusion

---

- In view of
  - 3 years positive results with hardware homework in a first year course for ECE students,
  - Promise of hardware homework to promote intensely interactive learning environments,
  - Success of prototype projects,
- ECE faculty voted to
  - Deploy hardware homework in first of restructured circuit and electronics courses in spring 2005
  - Strengthen labs in successive courses in view of stronger student lab experience in early courses